
**MIDDLE EAST TECHNICAL
UNIVERSITY**

**DEPARTMENT OF ELECTRICAL AND
ELECTRONICS ENGINEERING**

EE464 Simulation Project #2

April 20, 2018

Student 1: Mert KARAÇELEBİ - 2030930

Student 2: Tuna YILDIZ - 2031656

Student 3: Göksenin Hande BAYAZIT - 2093441

Contents

1	Introduction	1
2	Isolated Converter Design	1
2.1	Steady State Operation	1
2.2	Transformer Design	4
2.3	Discontinuous Mode Calculations	5
2.4	Non Ideal Simulation	7
2.5	Efficiency	10
2.6	Component Selection	14
2.6.1	Transformer	15
2.6.2	Capacitor	15
2.6.3	Diode	15
2.6.4	Switching Equipment	15
2.6.5	Rectifier Bridge	16
2.6.6	Analog Controller	16
3	Controller Design Using Buck Converter Topology	16
3.1	Analytic Transfer Function Calculations	16
3.2	Simulations	18
3.3	Type II Controller	19
3.4	Performance Analysis	20
3.5	Comments	21
4	Controller Design Using Flyback Converter Topology	21
4.1	Analytic Transfer Function Calculations	21
4.2	Simulations	22
4.3	Type II Controller	22
4.4	Performance Analysis	22
4.5	Comments	22
5	Conclusion	22
6	Appendix-A	22

1 Introduction

For EE464 (Static Power Conversion II) course hardware project has been announced. Our group "EMI Monster" selects flyback converter design with specified conditions given in Table 1.

Table 1: My caption

Project No	Vin (V)	Vout (V)	Pout (W)	Topology
9	230 AC	15	15	Flyback

We choose this project because flyback topology is more feasible to apply because of it does not require additional output inductance and third transformer winding to discharge magnetizing current. Moreover, our project needs to deal with high voltages but our load power is smaller than other projects therefore, overall design should require smaller components. In this report we have explained our design guide for project and simulation results for different cases.

2 Isolated Converter Design

2.1 Steady State Operation

In part a we were asked to implement the converter which converts 230 V_{rms} to 15 V output DC voltage. For this purpose, we implemented flyback converter. In flyback converter we used transformer and we adjusted the turns ratios of the transformer in order to have low voltage at the secondary side of the transformer. After that, by adjusting the duty cycle we obtained the 15 V output DC voltage. The circuit schematic of the flyback is in figure 1.

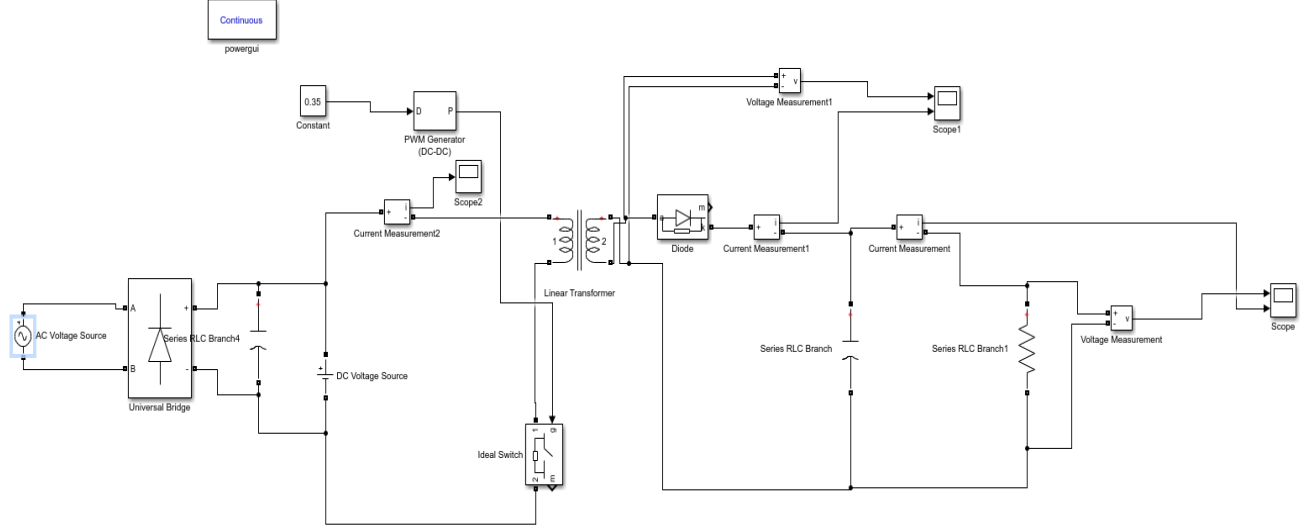


Figure 1: Flyback Converter Circuit Schematic

In flyback converter, in order to have an small magnetizing inductance value of the transformer for staying in continues conduction mode at normal operation, we decided the frequency of switch as 80 kHz. In other words, size of the transformer decreases as switching frequency increases. Moreover, with increasing switching frequency, all components such as filters, capacitors and inductors. However, when the switching frequency increases the switching loss increases as well.

In order to obtain the proper duty cycle value we used the formula 1

$$[H]V_o = V_{in} \times \frac{N_s}{N_p} \times \frac{D}{1-D} \quad (1)$$

By using this formula we calculated the D value as 0.35. While calculating the duty cycle we used the turns ratio of the transformer as calculated in the section 2.2.

Moreover, we are using the full bridge rectifier and DC link capacitor in order to have the DC voltage at the input of the flyback converter. For this purpose we calculated the input voltage of the flyback converter by using the formula 2.

$$V_{dc} = 0.9 \times V_{rms} \quad (2)$$

By using the formula 2 the V_{in} voltage of the flyback converter is calculated as the 207 V.

The output voltage and output current graph of the flyback converter that we designed in the project is in figure 2.

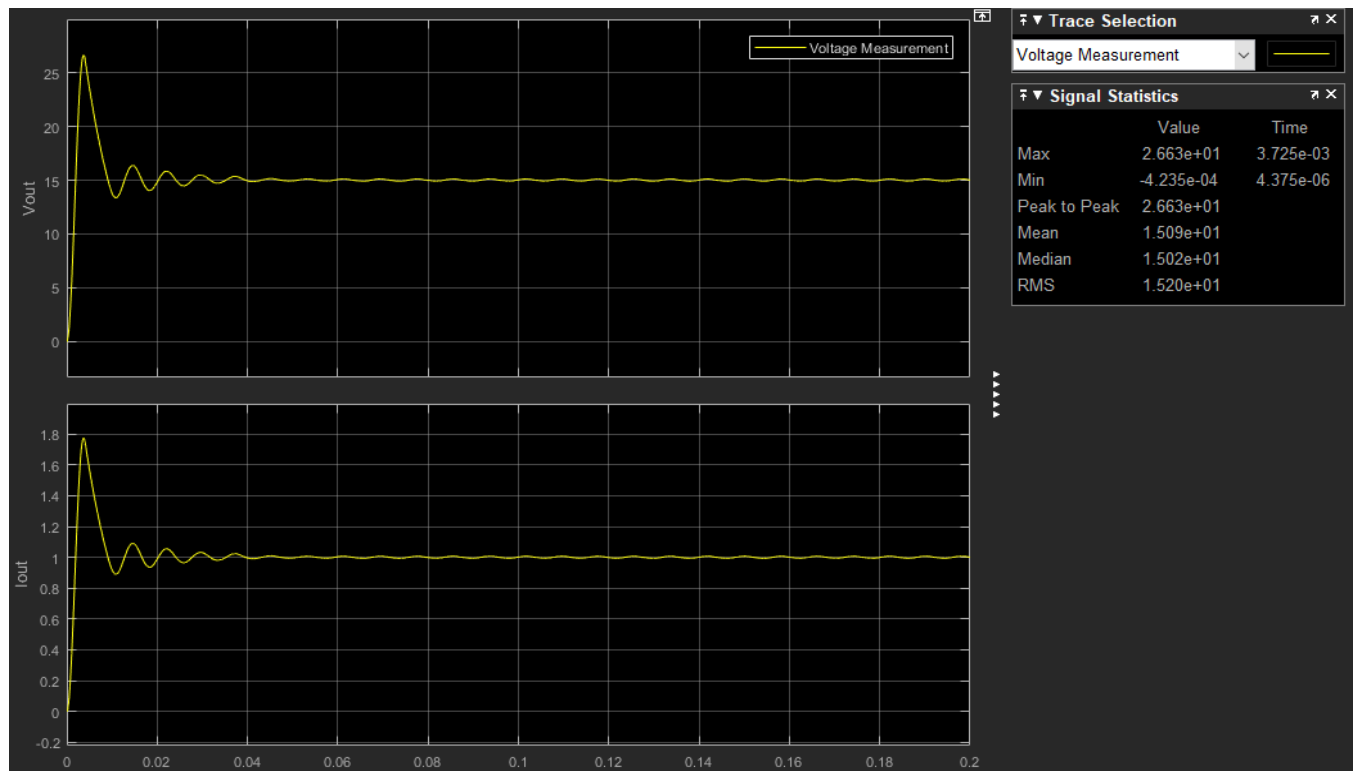


Figure 2: Output voltage and current graphs of the flyback converter.

2.2 Transformer Design

In this part we were asked to design a transformer. In order to design a transformer first we decided to geometry of the transformer and we selected the E shape core. After selecting the geometry of the transformer we decided to size of it. While deciding the shape of the transformer, we considered flyback switching frequency and the output power of the converter. Since our design has 15W power at the output at full load, we chose transformer which can operate well for 15W power. Chosen transformer is CF 139/E Core transformer. The transformer details are;

- Base Material of the transformer is MnZn
- Flux density at $25C^\circ$ is 490 mT
- Resistivity is $8\ m\Omega$

Also the data sheet of the transformer can be found in appendix section.

After choosing the transformer type, turns ratio of the transformer was decided. In order to find the turns ratio we used the formula 3.

$$\frac{V_o}{V_{in}} = \frac{D}{1-D} \times \frac{N_2}{N-1} \quad (3)$$

Before using the formula 3, we chose the duty cycle as 0.35. In that way we found the turns ratio as "7:1" for the flyback converter. With these calculated duty cycle and turns ratio we obtained the minimum magnetizing inductance value by using formula 4.

$$L_{min} = \frac{(1-D)^2 \times R}{2 \times f} \cdot \frac{N_1^2}{N_2} \quad (4)$$

$$L_{min} = \frac{(1-0.35)^2 \times 30}{2 \times 80kHz} \cdot \frac{7^2}{1} = 2.14mH$$

Also, in order to find how much we wind the primary and secondary windings of transformer we used the formula 5.

$$N_p > \frac{L_p \times I_{p,max}}{B_{sat} \times A_e} \quad (5)$$

Since our core's $A_e = 125mm^2$ and $B_{sat} value is = 0.3T$. We found turns number as;

- $N_p = \frac{2.14mH \times 0.145}{25mm^2 \times 0.3T} \approx 42$
- $N_s = N_p/7 \approx 6$

After all calculations we obtained the equivalent circuit parameters of the transformer. In other words, we are able to make an other calculations by considering those parameters.

2.3 Discontinuous Mode Calculations

Discontinuous mode is defined for flyback converter as; magnetizing current of transformer drops to zero in one cycle period. This condition is directly related to duty cycle of switching and inductance of the magnetizing branch. Magnetizing inductance can be found from the number of turns in the primary winding. This magnetizing inductance is calculated in 8.

$$L_{min} = \frac{(1 - D)^2 \times R}{2 \times f} \cdot \frac{N_1^2}{N_2} \quad (6)$$

We have designed our converter to operate at continuous mode when loading is 50%. Our nominal load is 15 Ohm. In our minimum magnetizing inductance calculation we calculated with 30 Ohm. As stated before our turns ratio is 7 (N1/N2), duty cycle is 0.35 (D) and switching frequency is 80 kHz (f).

$$L_{min} = \frac{(0.65)^2 \times 30}{2 \times 80000} \cdot \frac{7^2}{1} = 2.14mH \quad (7)$$

We expect to observe discontinuous mode of operation at higher resistances/ lower load currents than %50 loading case. Minimum current of magnetizing branch can be calculated in equation . Naturally at the edge of discontinuous minimum magnetizing current should be zero.

$$I_{min} = I_{lm} - \frac{\Delta I_{lm}}{2} \quad (8)$$

$$I_{min} = \frac{V_s \times D}{(1 - D)^2 \times R} \times \left(\frac{N_1}{N_2}\right)^2 - \frac{V_s \times D \times T_s}{2 \times L_m} \quad (9)$$

Using equation 9 we calculated the R value as:

$$R = \frac{2 \times L_m}{(1 - D)^2 \times T_s} \times \left(\frac{N_1}{N_2}\right)^2 = 29.98\Omega \quad (10)$$

This result is expected. In figure 3 one can find the simulation results for 30 Ohm load in secondary side of the transformer. In 30 Ohm load our minimum current for continuous operation is 0.5 A . In figure 4 shows the load current and voltage.

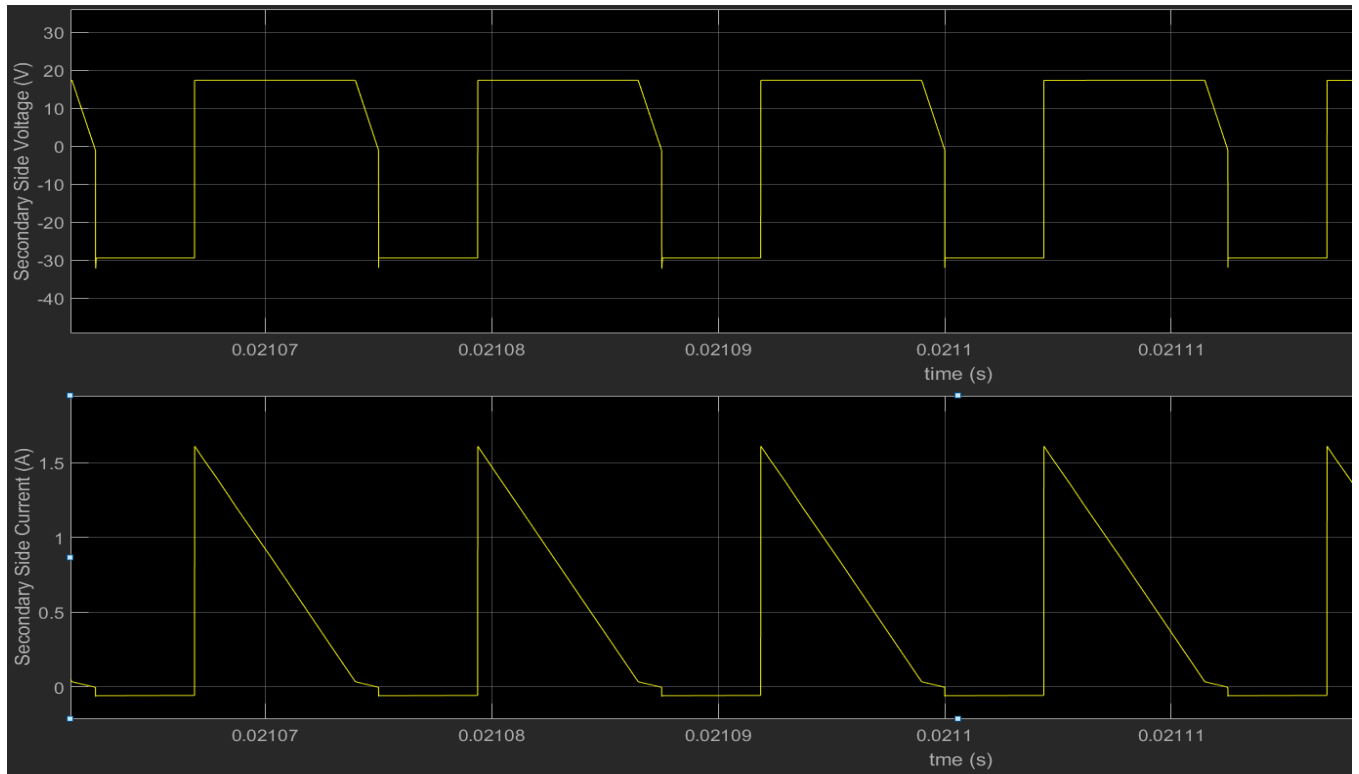


Figure 3: Transformer Secondary Side Voltage and Current Waveform

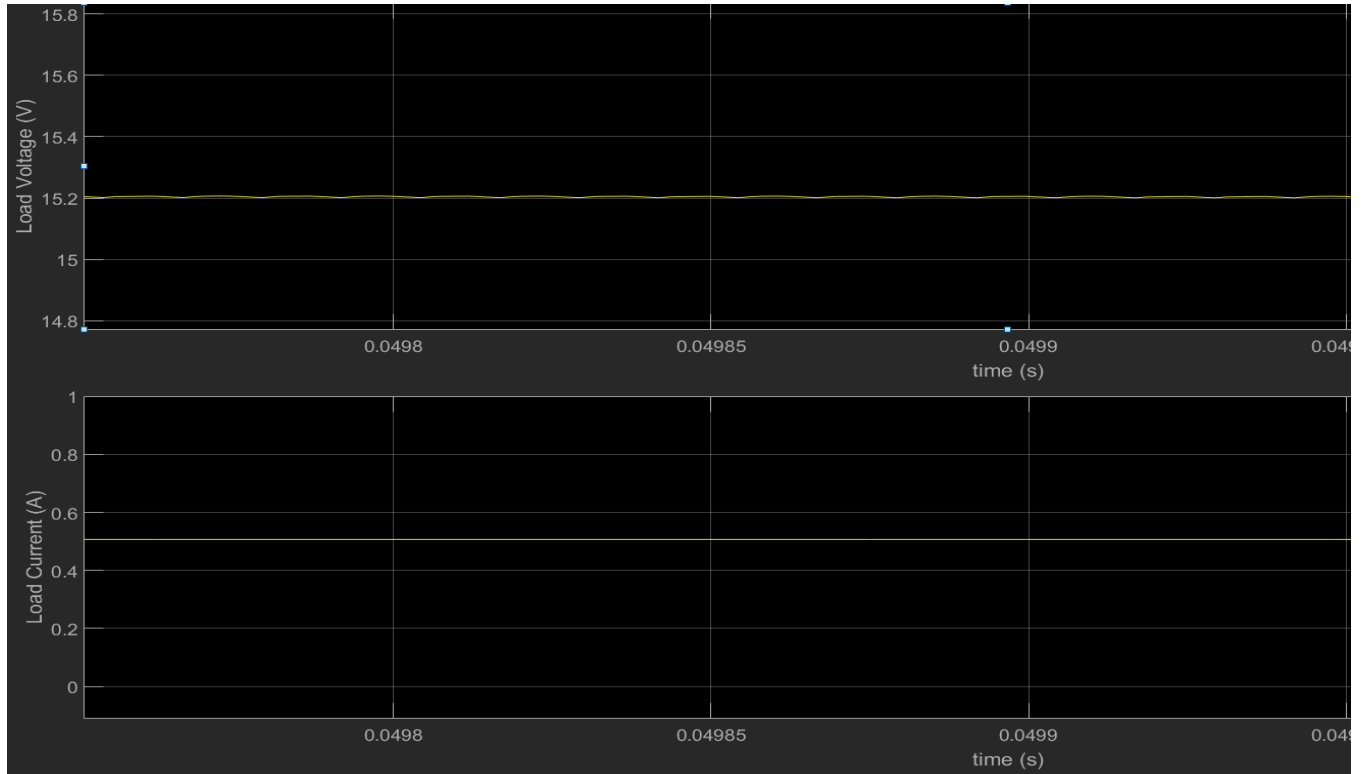


Figure 4: Load Voltage and Current Waveform at the Edge of Discontinuous

Our normal operation is shown in section 2.1. When we increased the load resistance 1 Ohm more we observed sudden voltage drop at the secondary terminals while switch is still operating at off condition. This kind of operation is not desired using a controller can solve this issue since our design is capable to compensate the increment in duty cycle up to 0.5 approximately.

2.4 Non Ideal Simulation

In this circuit we were asked to implement the same flyback converter with using the non ideal switches. The circuit schematic is in figure 5.

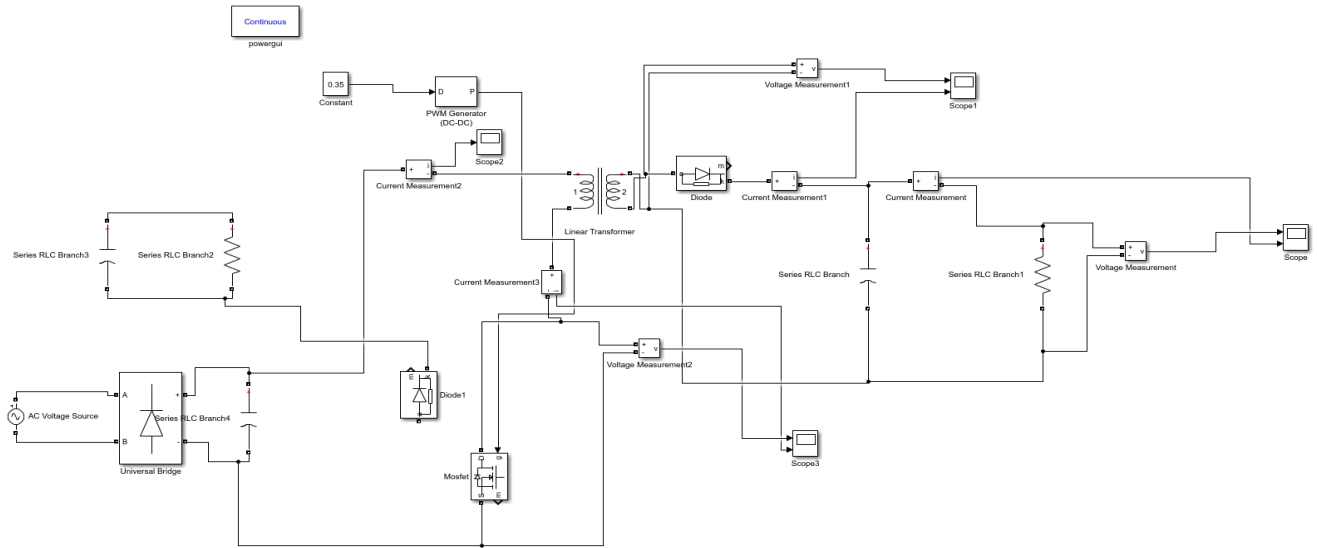


Figure 5: The circuit schematic with non ideal switches and without snubber circuit.

The switch voltage and current graph is in figure 6.

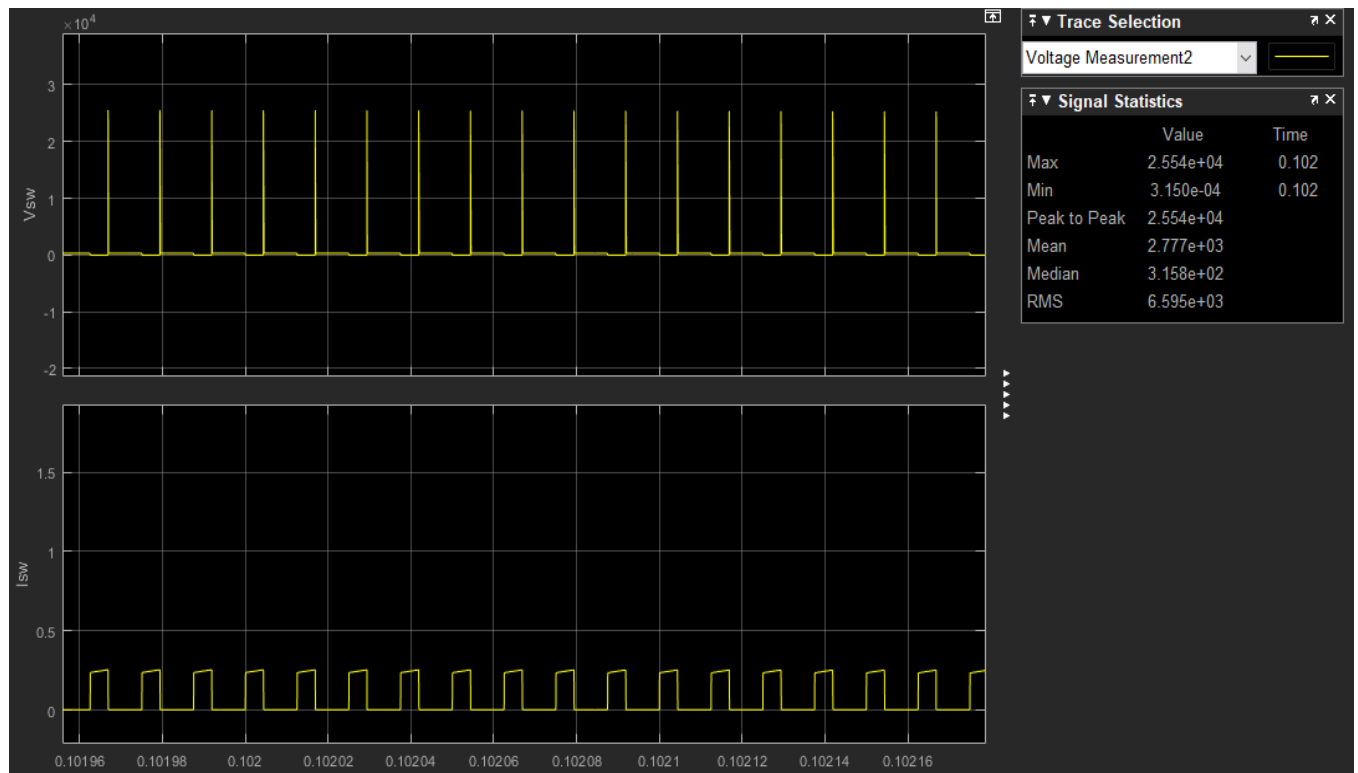


Figure 6: The switch voltage and switch current graph of the flyback converter.

As it seen from the figure 6 when we use the non ideal switch and not using the snubber

circuit, voltage is increasing to 2.5444×10^4 . It is serious problem for the switch component since it sees very high voltage when the switch is off. Therefore, we need the snubber circuit for protect the switch from high voltages.

The flyback converter with the snubber circuit is in figure 7.

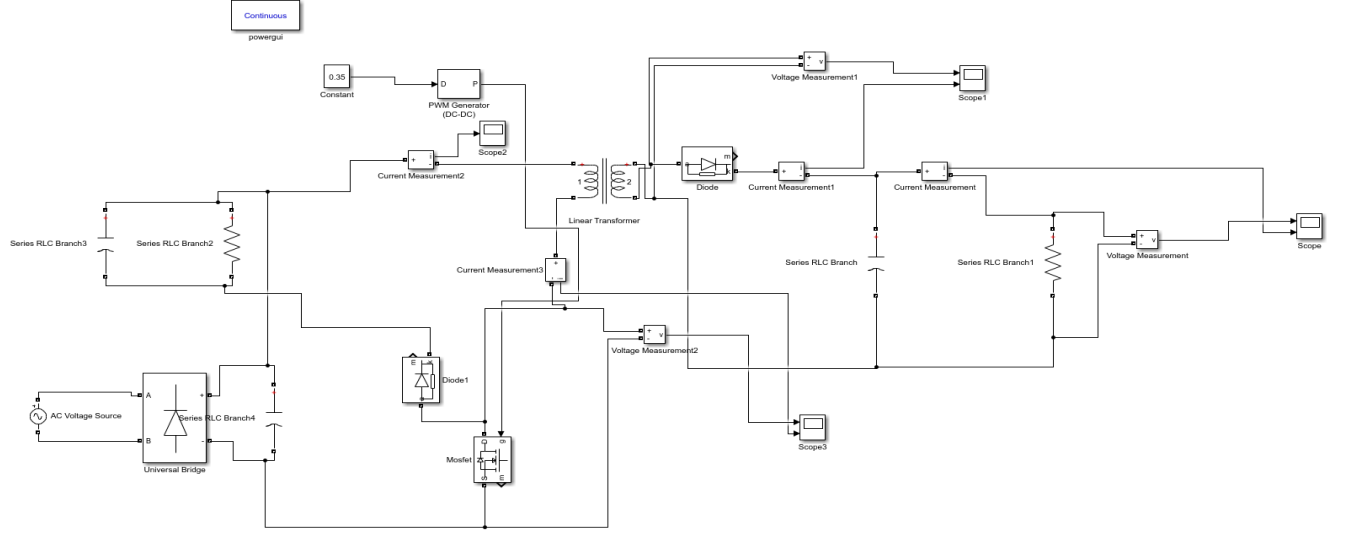


Figure 7: The flyback converter with snubber circuit.

The voltage and current of the switch graph is in figure 8.

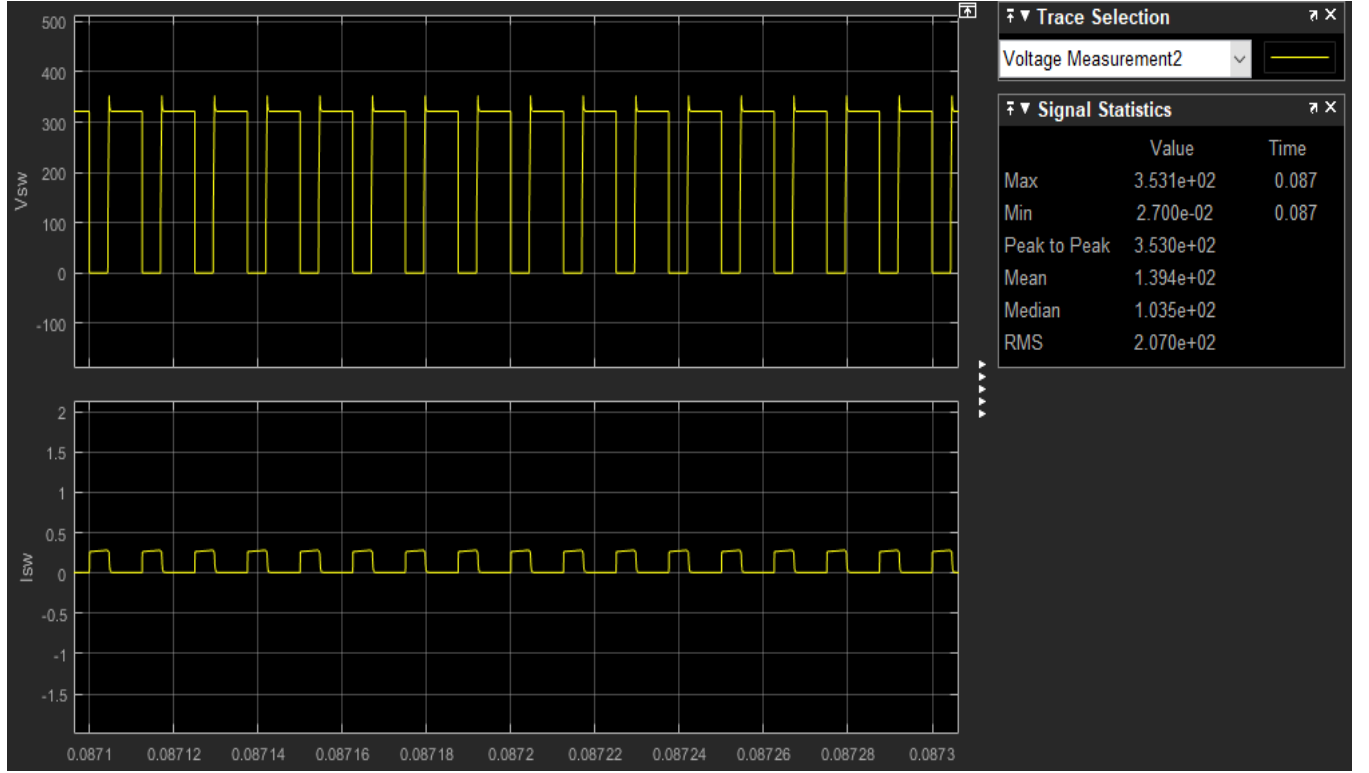


Figure 8: The voltage and current graph of the switch.

As is seen from the figure 6 and 8 there is quite difference for voltage being seen at the switch. Therefore, we built a snubber circuit for reducing the overshoots for switch voltages. In order to have a proper snubber circuit we used some equations which are 11, 12.

$$C > \frac{V_{clamp}}{V_{ripple} \times f_{sw} \times R} \quad (11)$$

$$R < 2 \times V_{clamp} \times \frac{V_{clamp} - V_{OR}}{L_{leak} \times I_p^2 \times f_{sw}} \quad (12)$$

By using these 11 and 12 formulas we obtained the resistance value as $75 \text{ k}\Omega$ and capacitance value as 330 pF .

2.5 Efficiency

In this section we were asked to calculate the efficiency of the flyback converter that we designed during the project. In order to calculate the efficiency we used the formula 13.

$$\delta = \frac{V_o \times I_o}{V_{in} \times I_{in}} \quad (13)$$

By using voltage and current graph we calculate the efficiency. The voltage and current graph for full load is in 9, 75% load is in 10, 50 % load is in 11, 25 % load is in 12.

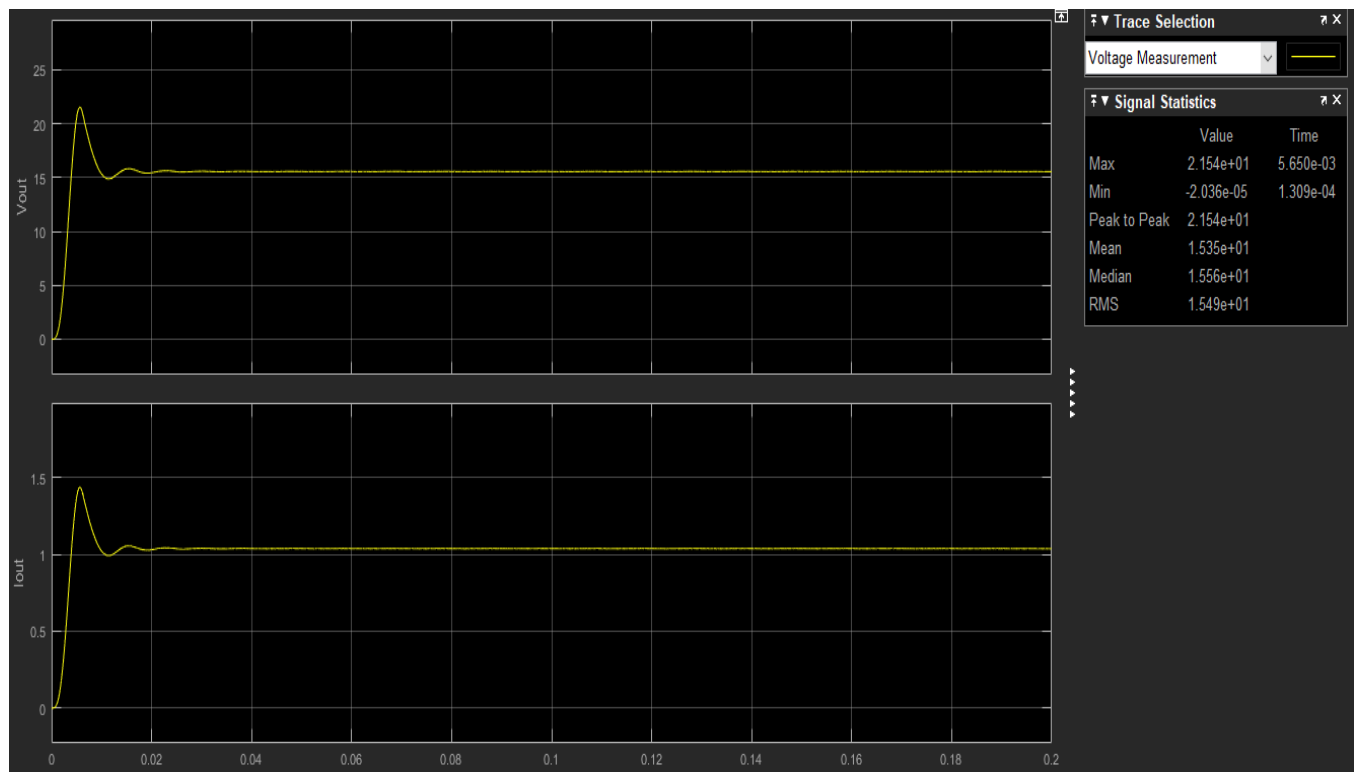


Figure 9: The voltage and current graph of the full load.

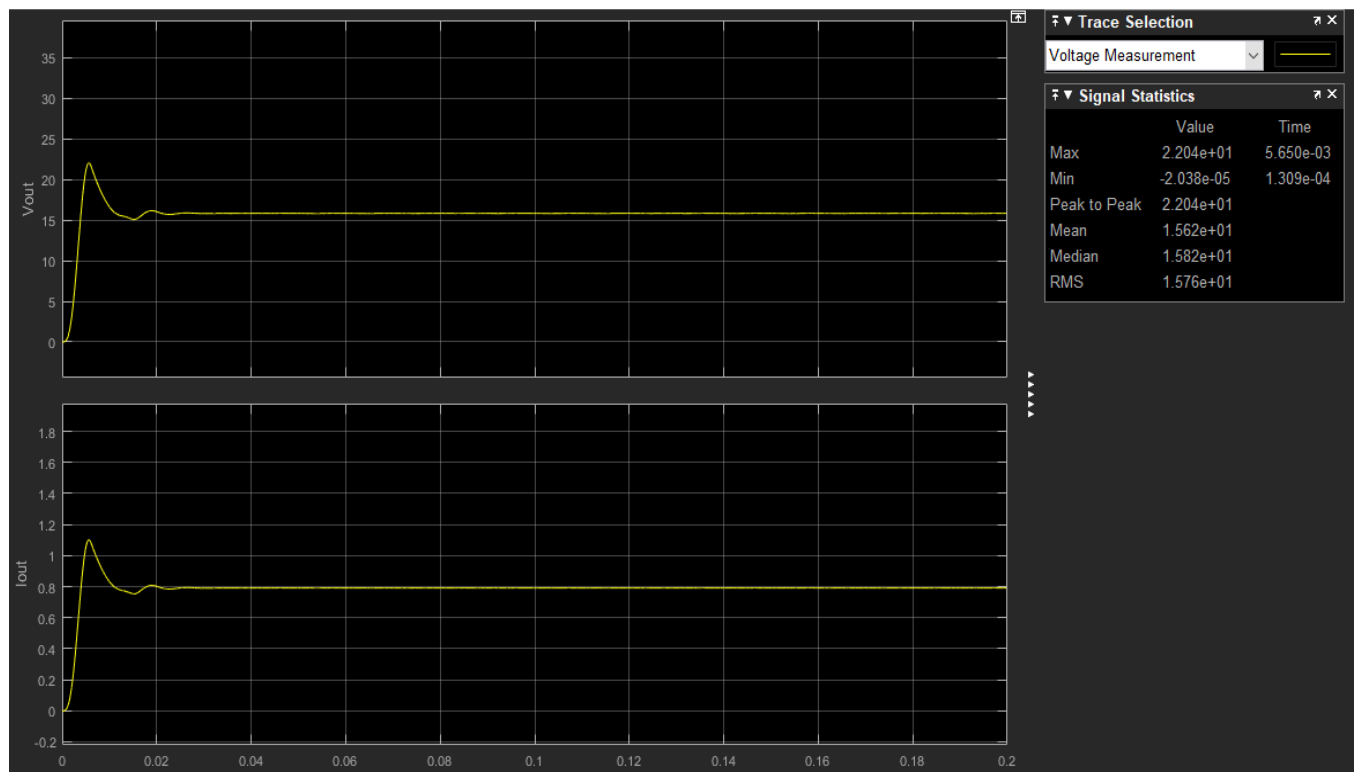


Figure 10: The voltage and current graph of the 75 % load.

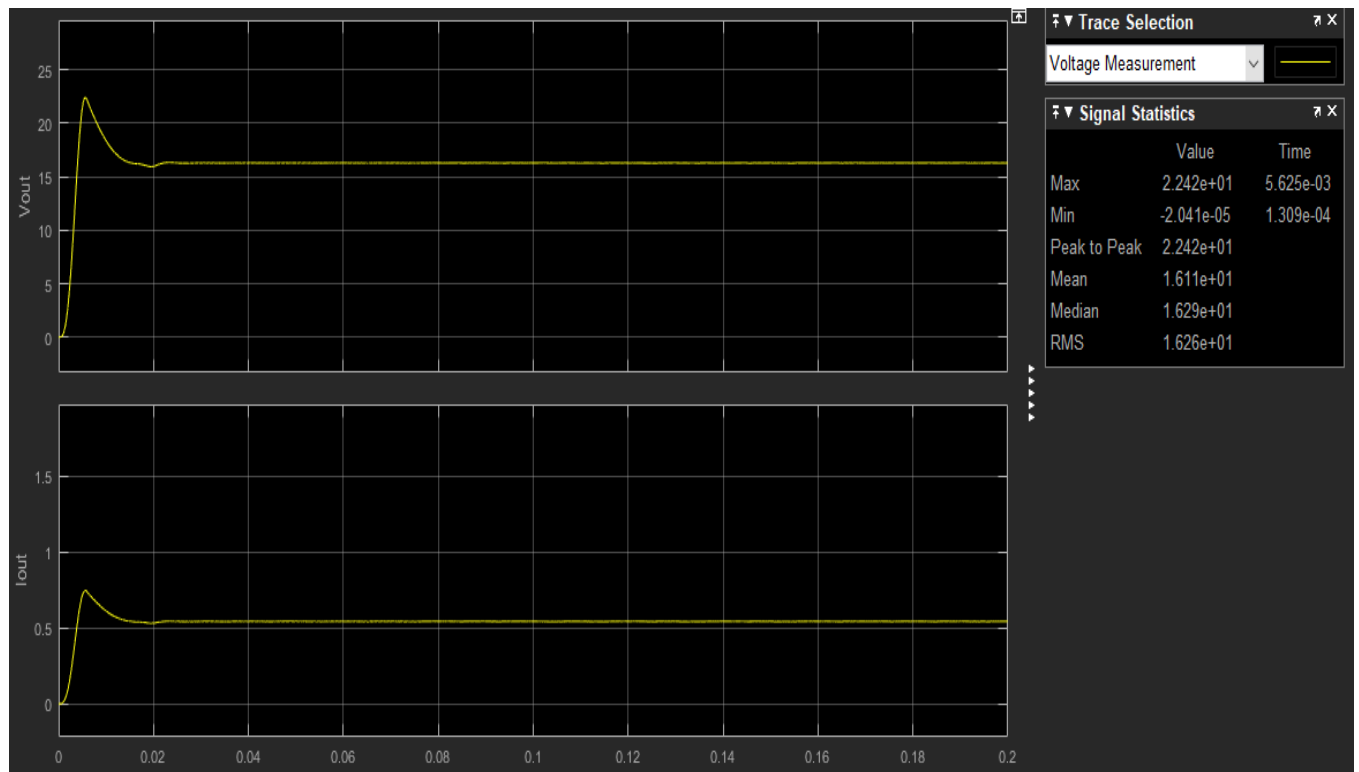


Figure 11: The voltage and current graph of the 50 % load.

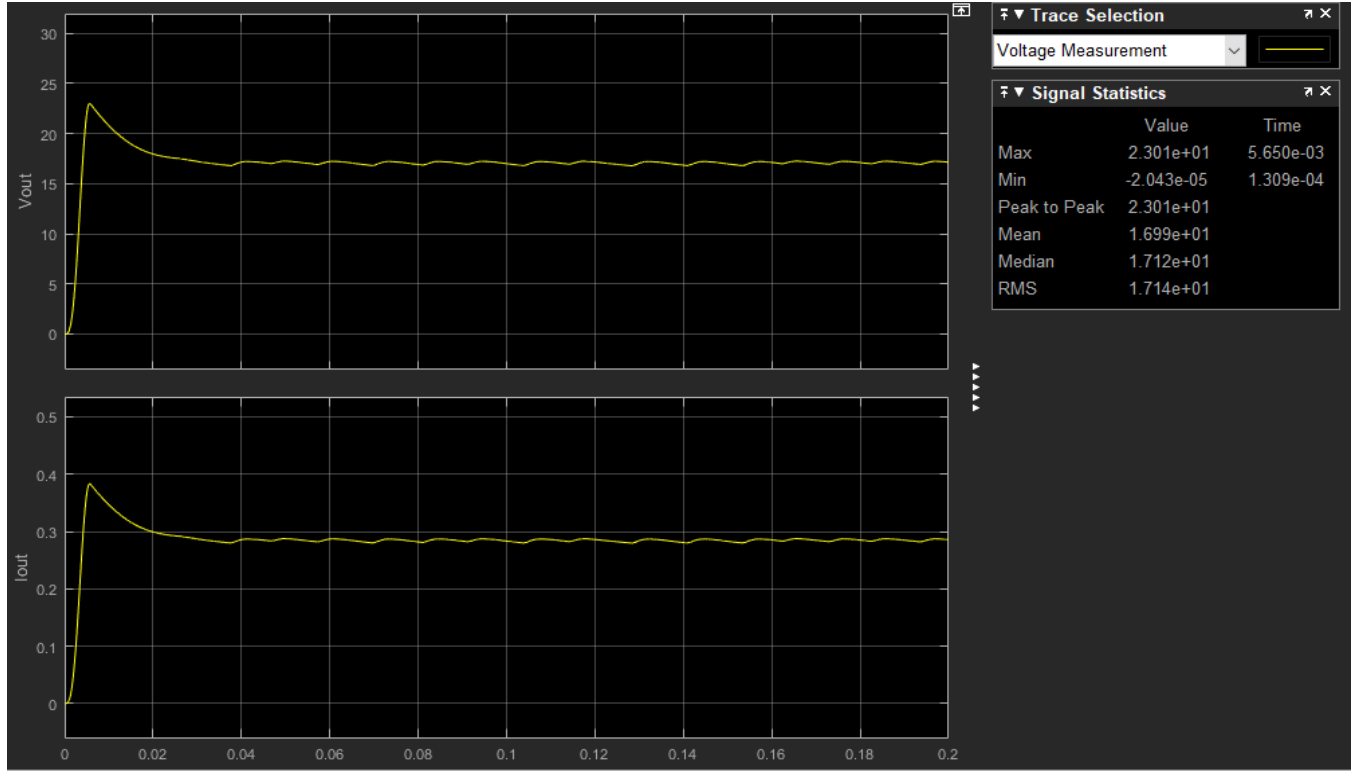


Figure 12: The voltage and current graph of the 25 % load.

The efficiency values are;

$$\begin{aligned}\delta_{fullload} &= \frac{15 \times 1}{207 \times 0.81} = \%40 \\ \delta_{\%75load} &= \frac{15 \times 0.75}{207 \times 0.14} = \%38 \\ \delta_{\%50load} &= \frac{15 \times 0.5}{207 \times 0.11} = \%32 \\ \delta_{\%25load} &= \frac{15 \times 0.25}{207 \times 0.058} = \%31\end{aligned}$$

2.6 Component Selection

For this project we add every component a safety margin with all those margins our component list has been found at table ?? . All of these components have already been bought, on the other hand if unexpected situations are encountered we could change our components during the implementation part of the project.

2.6.1 Transformer

Transformer design is the most important part of this project. We have already calculated the core size, turns ratio and primary turn number in transformer design section. This calculations are made on power ratings and magnetizing current rate. Since our transformer should capable of transferring 15 Watts of power, we selected ferrite CF139 E core. Details of core is explained in section 2.2, related data sheet can be found in appendix.

2.6.2 Capacitor

We need two different capacitor for primary and secondary side of the transformer. At the exit of 1 phase diode rectifier we need a DC Link capacitor in order to obtain ripple free DC voltage. For secondary side we need low pass filter capacitor. In table ??, one can find the specifications of the capacitors.

Table 2: Capacitor Information

Component	Model	I rated (A)	Vrated (V)	Value
Capacitor	CD60	-	330	600 uF
Capacitor	CD110X	-	35	100 uF

2.6.3 Diode

For flyback converter diode roles as a blocker for the period duty on, current rating and blockage voltage rating should be similar to output characteristics. In table 3, one can find the diode information and in appendix A one can find the related data sheet. We choose fast diode in order to work at high frequencies.

Table 3: Diode Data

Component	Model	I forward (A)	Vblockage (V)
Diode	BYT 08P 1000	16	1000

2.6.4 Switching Equipment

Since we implement our design at working under high frequencies, the best switching device could be Mosfet for this kind of operation. IRF820 is selected for our design and this decision is made based on voltage rating, low switching loses and simple gate driver. In table 4 one can find the related information about our design. Snubber circuit is a compulsory for switching transformers magnetizing branch over-voltages to protect switching equipment.

Table 4: Switching Equipment Data

Component	Model	Id (A)	Vds (V)	ton+toff (ns)
Mosfet	IRF820	2.5	500	41

2.6.5 Rectifier Bridge

For supply we are using 230 V AC from grid. For flyback converter we rectify this signal with using full bridge diode rectifier. Ratings of rectifier is simple and it does not require any additional calculations. For this purpose we bought B80-C800 bridge rectifier.

Table 5: My caption

Component	Model	If (A)	Vdc (V)
Bridge Rectifier	B80-C5000	1.5	200

2.6.6 Analog Controller

Since this kind of converters should work under various loads we need a controller circuit to adjust the duty cycle of switching equipment. For this purpose we will use analog PID controller UC38448. This is a current sensing control device additional circuitry is required. Operation principle of this kind of controllers are described in detail in Section 3.

3 Controller Design Using Buck Converter Topology

3.1 Analytic Transfer Function Calculations

To calculate the transfer function analytically, we used linearization with state space averaging technique. Considering both modes of operation (switch ON and OFF periods), we obtained two state space systems and calculated the weighted average with respect to duty cycle. Obtained state-space system is as follows:

$$\begin{aligned}
 x &= \begin{bmatrix} v_C \\ i_L \end{bmatrix} \\
 \dot{x} &= \begin{bmatrix} \frac{-1}{RC} & \frac{1}{C} \\ \frac{-1}{L} & 0 \end{bmatrix} x + \begin{bmatrix} 0 \\ \frac{D}{L} \end{bmatrix} V_{in} \\
 y &= \begin{bmatrix} 1 & 0 \end{bmatrix} x
 \end{aligned}$$

Hence, the transfer function is obtained from this state space system as:

$$H(s) = \frac{\frac{D}{LC}}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

Replacing the values $C = 100\mu F$, $L = 0.1mH$, $R = 15\Omega$, $D = 0.075$, $H(s)$ becomes:

$$H(s) = \frac{7.5 \cdot 10^6}{s^2 + 666.7s + 10^8}$$

Bode plot of this transfer function is shown in Figure 13

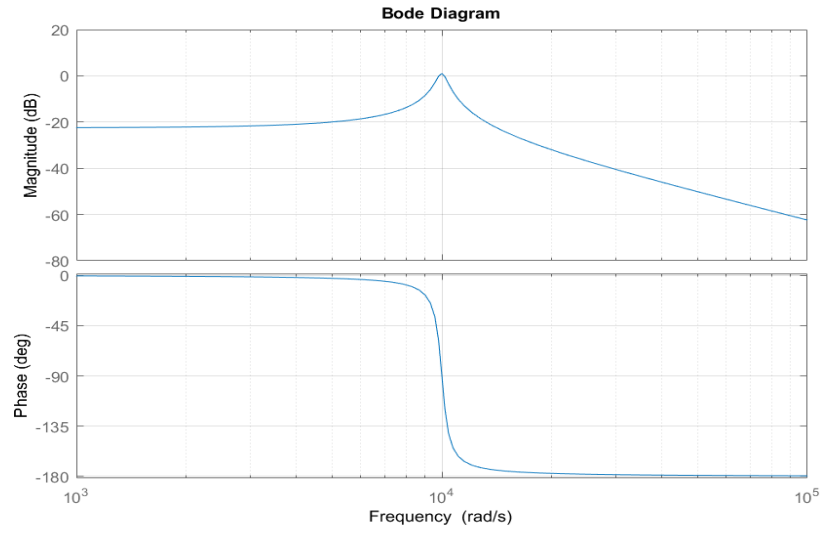


Figure 13: Bode Plot of Analytically Calculated Transfer Function

Obviously, the system is close to be unstable, as its phase margin decay rate is too large around 10 krad/s.

3.2 Simulations

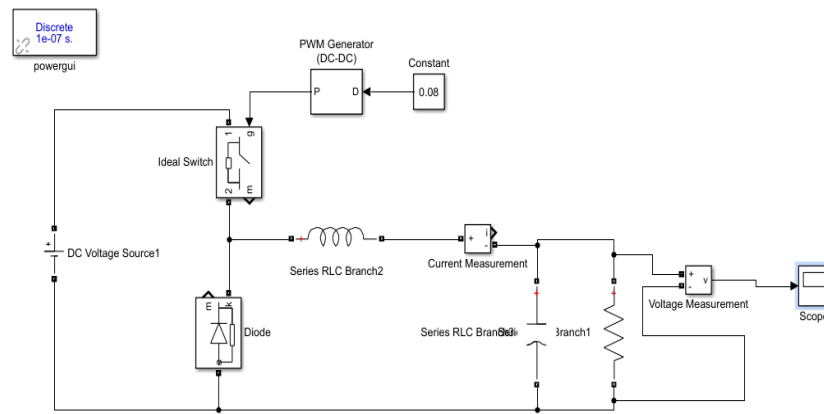


Figure 14: Buck Converter

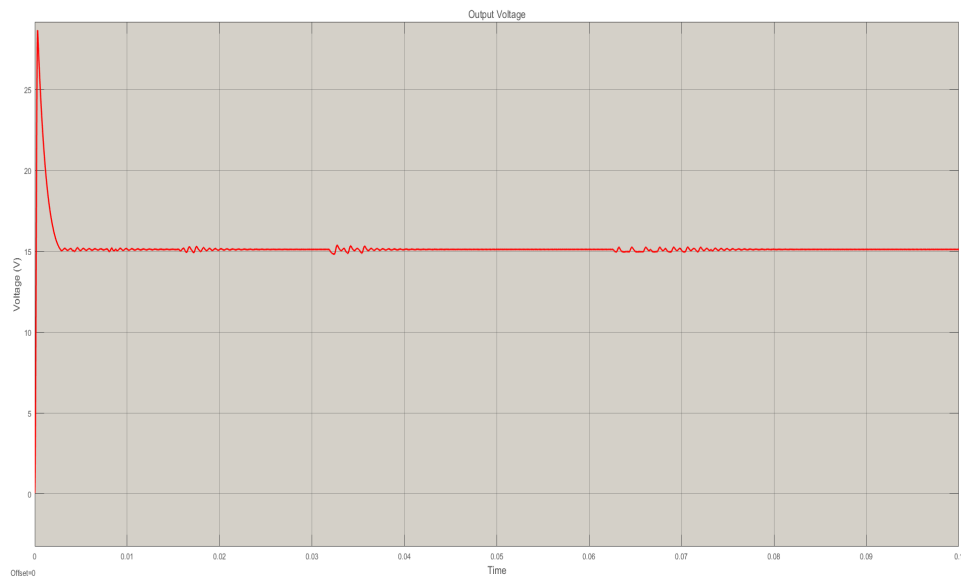


Figure 15: Output Voltage of Uncontrolled System

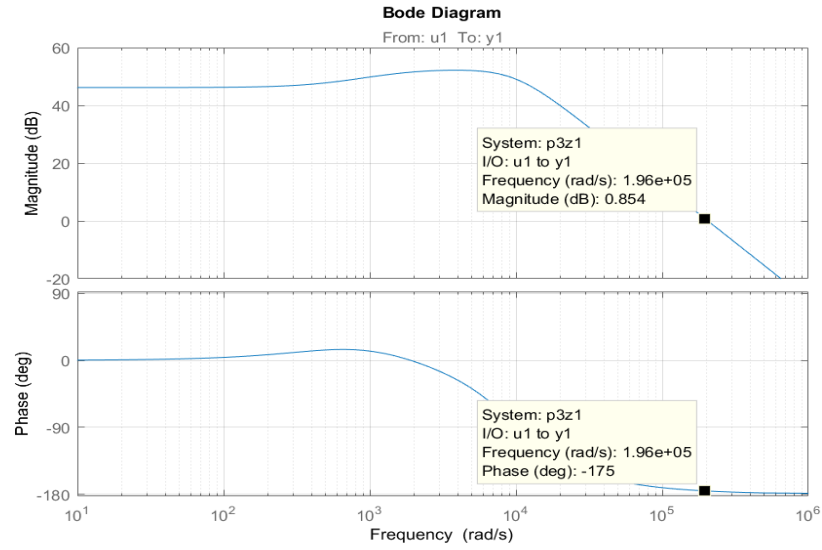


Figure 16: Bode Plot of Transfer Function Obtained with System Identification

3.3 Type II Controller

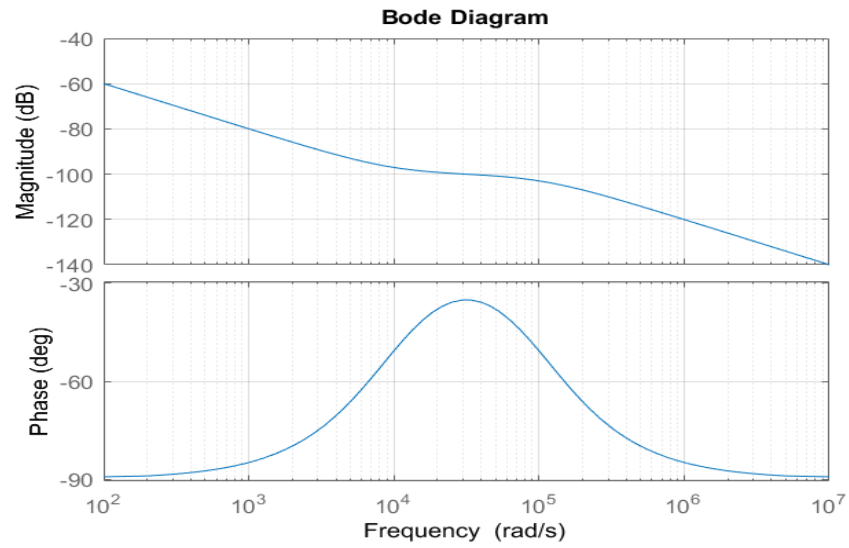


Figure 17: Bode Plot of Designed Controller

3.4 Performance Analysis

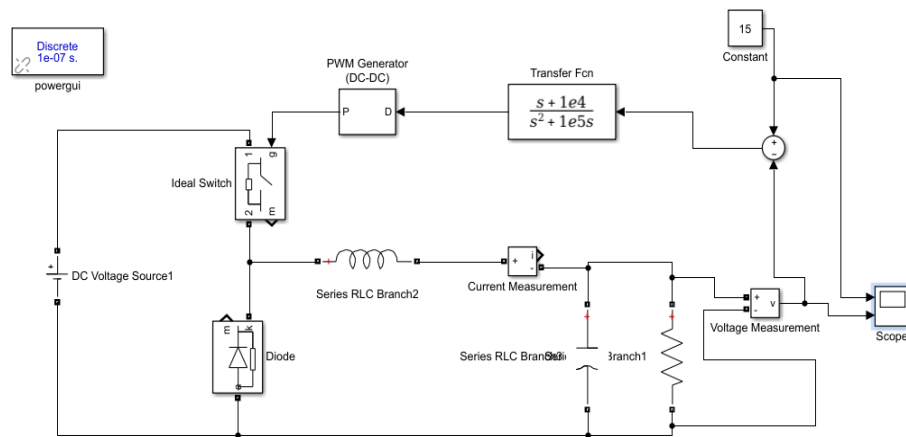


Figure 18: Controlled Buck Converter

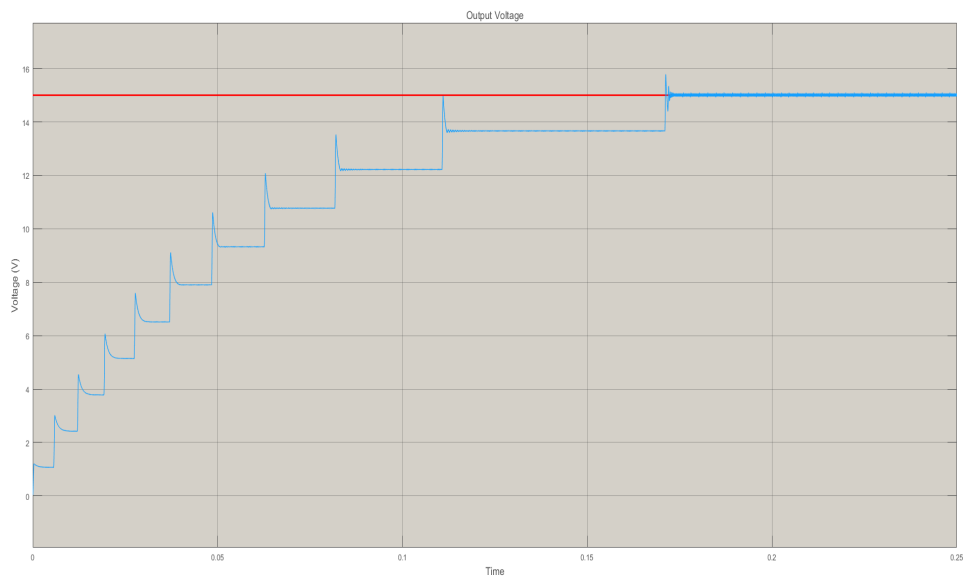


Figure 19: Output Voltage of Controlled System

3.5 Comments

4 Controller Design Using Flyback Converter Topology

4.1 Analytic Transfer Function Calculations

For analytical calculation of the transfer function of the flyback topology, we used linearization with state space averaging technique, again. Having obtained the state space matrices with respect to two states, we calculated the transfer function using MATLAB. State space matrices are as follows:

$$\begin{aligned}x &= \begin{bmatrix} v_C \\ i_L \end{bmatrix} \\ \dot{x}_1 &= \begin{bmatrix} \frac{-1}{RC} & 0 \\ 0 & 0 \end{bmatrix} x_1 + \begin{bmatrix} 0 \\ \frac{D}{L} \end{bmatrix} V_{in} \\ \dot{x}_2 &= \begin{bmatrix} \frac{-1}{RC} & \frac{7}{C} \\ \frac{-7}{L} & 0 \end{bmatrix} x_2 + \begin{bmatrix} 0 \\ 0 \end{bmatrix} V_{in} \\ y &= \begin{bmatrix} 1 & 0 \end{bmatrix} x\end{aligned}$$

Replacing the values $C = 600\mu F$, $L = 3.8mH$, $R = 15\Omega$, $D = 0.35$, $H(s)$ becomes:

$$H(s) = \frac{-2333s^3 + 2.11 * 10^8 s^2 + 2.317 * 10^9 s + 1.921 * 10^{15}}{s^4 + 222.2s^3 + 1.817 * 10^7 s^2 + 2.018 * 10^9 s + 8.245 * 10^{13}}$$

Bode plot of this transfer function is shown in Figure 20

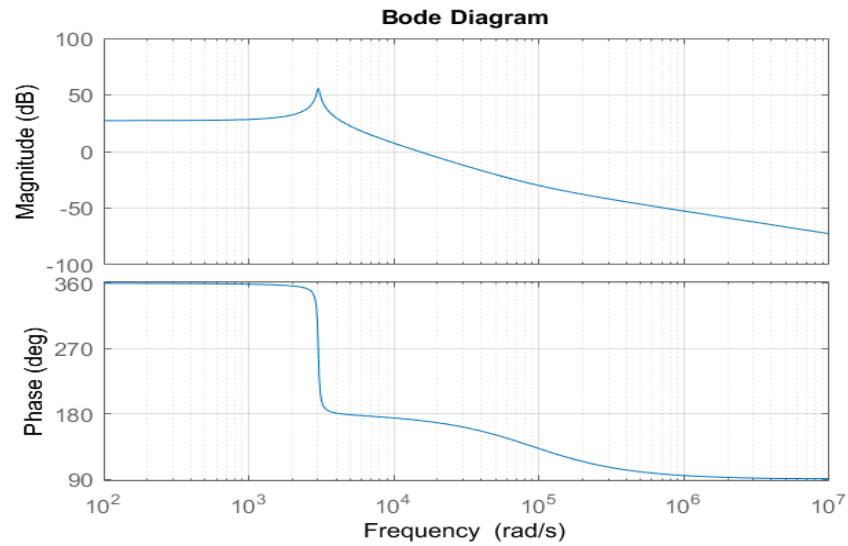


Figure 20: Bode Plot of Analytically Calculated Transfer Function

4.2 Simulations

4.3 Type II Controller

4.4 Performance Analysis

4.5 Comments

5 Conclusion

6 Appendix-A

Appendix A contains related data sheets of selected equipments in EE 464 Hardware project.

Mosfet: <https://www.vishay.com/docs/91059/91059.pdf>

Capacitor: <http://pdf1.alldatasheet.com/datasheet-pdf/view/340635/SUNTAN/TS13D3-CD60.html>

<http://www.ersinelektronik.com/class/INNOVAEditor/assets/Datasheets/Elektrolitik-Radial.pdf>

Diode Bridge: <https://www.digchip.com/datasheets/parts/datasheet/139/B80-C1500R-pdf.php>

Diode: <http://pdf.datasheetcatalog.com/datasheet/SGSThompsonMicroelectronics/mXrxyqv.pdf>

Transformer Core: <http://www.cosmoferrites.com/Downloads/Alnh/CF139.pdf>